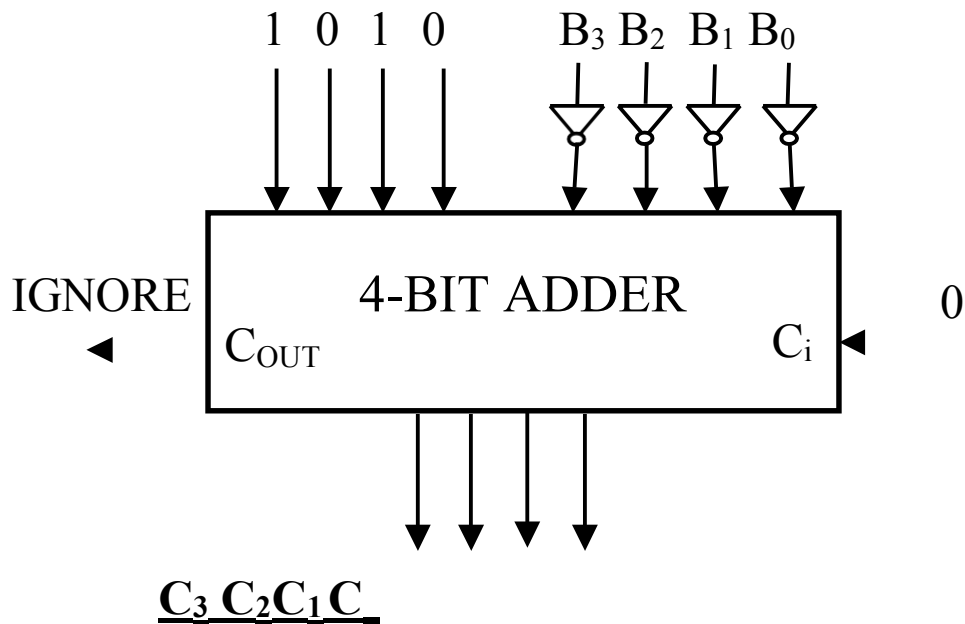


EXERCISE

DESIGN A 9's COMPLEMENT
GENERATOR FOR A BCD DIGIT:



Read the following notes before
starting the exercise!!!

BINARY CODED DECIMAL: **B.C.D.**

- ANOTHER METHOD TO REPRESENT DECIMAL NUMBERS
- USEFUL BECAUSE MANY DIGITAL DEVICES PROCESS + DISPLAY NUMBERS IN TENS

IN **BCD EACH** NUMBER IS DEFINED BY A BINARY CODE OF **4 BITS**.

***** 8 – 4 – 2 – 1 MOST COMMON CODE**

8 – 4 – 2 – 1 CODE INDICATES THE WEIGHT OF EACH BIT $2^3 - 2^2 - 2^1 - 2^0$

E.G. 934 = 1001 0011 0100
9 3 4

FOR **EACH** DIGIT A **BINARY** [NORMAL] **CODE** IS ALLOCATED.

OTHER REPRESENTATION FORMS ARE **2-4-2-1** AND **EXCESS-3**

BINARY	8-4-2-1	2-4-2-1	EXCESS-3
0000	0	0	NOT USED
0001	1	1	NOT USED
0010	2	2	NOT USED
0011	3	3	0
0100	4	4	1
0101	5	NOT USED	2
0110	6	NOT USED	3
0111	7	NOT USED	4
1000	8	NOT USED	5
1001	9	NOT USED	6
1010	NOT USED	NOT USED	7
1011	NOT USED	5	8
1100	NOT USED	6	9
1101	NOT USED	7	NOT USED
1110	NOT USED	8	NOT USED
1111	NOT USED	9	NOT USED

- WE WILL USE 8-4-2-1 BCD
- DECIMAL NUMBERS > 9 MAY BE OBTAINED WHEN ADDING TWO DECIMAL DIGITS (RANGE: 0-18)
I.E. $0 + 0 \div 9 + 9$. ONLY $0 \rightarrow 9$ HAVE THE CORRECT BCD CODE.
- WE NEED TO CORRECT THE OTHERS

DECIMAL	UNCORRECTED BCD SUM $C_3' S_3' S_2' S_1' S_0$	CORRECTED BCD SUM $C_N S_3 S_2 S_1 S_0$
0	0 0 0 0	0 0 0 0
:	:	:
9	1 0 0 1	1 0 0 1
10	1 0 1 0	1 0 0 0 0
11	1 0 1 1	1 0 0 0 1
12	1 1 0 0	1 0 0 1 0
13	1 1 0 1	1 0 0 1 1
14	1 1 1 0	1 0 1 0 0
15	1 1 1 1	1 0 1 0 1
16	1 0 0 0 0	1 0 1 1 0
17	1 0 0 0 1	1 0 1 1 1
18	1 0 0 1 0	1 1 0 0 0
19	1 0 0 1 1	1 1 0 0 1

- **0→9 ONLY LEGAL CODES**

E.G. 19 = 1 9 = 0001 1001 = 11001

THUS, FOR SUMS BETWEEN **10 → 18** MUST
SUBTRACT 10 AND PRODUCE A CARRY

SUBTRACT 10 = 1010_2 >> **ADD 2's**
COMPLEMENT = 0110

4-BIT BCD ADDER

TO ADD TWO DIGITS

FOR SUMS >9 WE NEED TO ADD 2's
COMPLEMENT of 10_{10} TO THE
UNCORRECTED RESULT ($S'_3 S'_2 S'_1 S'_0$)

CORRECTION IS **ALSO** NEEDED WHEN
A **CARRY OUT** (C'_3) IS GENERATED
[NUMBERS $16 \rightarrow 18$]

**>>>> A DECODER IS REQUIRED TO
DETECT WHEN CARRY OUT (C_N) TO
THE NEXT STAGE IS NEEDED**


K-MAP FOR C_N

		$S'_1 S'_0$			
		0 0	0 1	1 1	1 0
$S'_3 S'_2$	0 0	0	1	3	2
	0 1	4	5	7	6
	1 1	12	13	15	14
	1 0	8	9	11	10

>>>> $C_N = C'_3 + S'_3 S'_2 + S'_3 S'_1$

TO IMPLEMENT A 4 BIT BCD ADDER WE NEED TWO 4-BIT FULL ADDERS, ONE TO ADD TWO 4-BIT BCD NUMBERS AND THE OTHER FULL ADDER TO ADD 2's COMPLEMENT OF 10_{10} TO THE RESULT IF $C_N = 1$

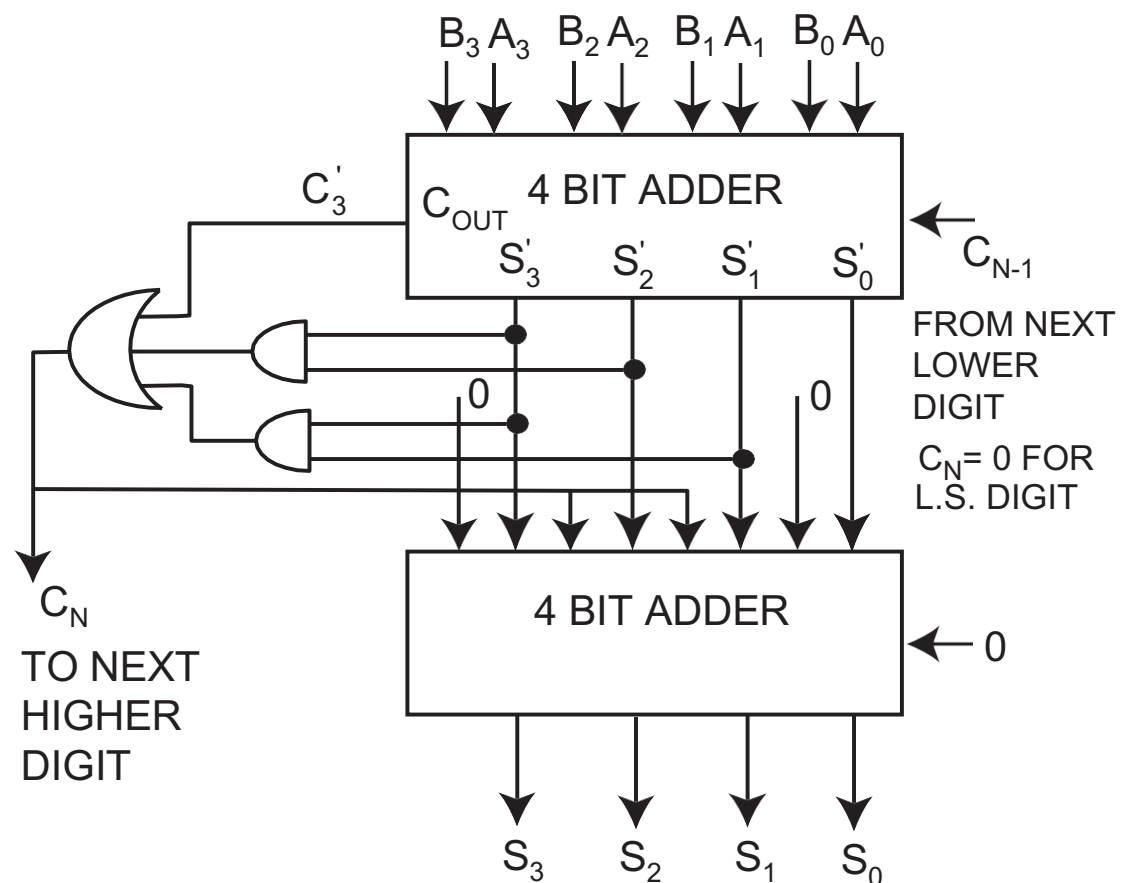ALSO WE NEED 2 AND GATES AND ONE OR GATE TO GENERATE C_N



- ADD 0110 WHEN $C_N=1$
- ADD 0000 WHEN $C_N=0$

BCD SUBTRACTION

9's COMPLEMENT

THE 9's COMPLEMENT OF A DECIMAL NUMBER IS FOUND BY SUBTRACTING EACH DIGIT IN THE NUMBER FROM 9

DECIMAL DIGIT	9's COMPLEMENT
0	9
1	8
2	7
!	!
.	.
9	0

E.G. 9's COMPLEMENT of 28 = $99 - 28$
= 71

9's COMPLEMENT of 562 = $999 - 562$
= 437

SUBTRACTION OF A SMALLER DECIMAL NUMBER FROM A LARGER ONE CAN BE DONE BY ADDING THE 9's COMPLEMENT OF THE SMALLER NUMBER TO THE LARGER NUMBER AND THEN ADDING THE CARRY TO THE RESULT (END AROUND CARRY).

WHEN SUBTRACTING A LARGER NUMBER FROM A SMALLER ONE THERE IS **NO CARRY** AND THE **RESULT** IS IN **9's COMPLEMENT FORM** AND **NEGATIVE**.

EXAMPLES:

(a)
$$\begin{array}{r} +8 \\ -3 \\ \hline 5 \end{array}$$

$$\begin{array}{r} +8 \\ +6 \leftarrow \text{9's COMP. OF 3} \\ \hline (1) 4 \\ \rightarrow +1 \quad \text{END AROUND CARRY} \\ \hline 5 \end{array}$$

(b)
$$\begin{array}{r} 54 \\ -21 \\ \hline 33 \end{array}$$

$$\begin{array}{r} 54 \\ 78 \leftarrow \text{9's COMP. OF 3} \\ \hline (1) 32 \\ \rightarrow +1 \quad \text{END AROUND CARRY} \\ \hline 33 \end{array}$$

(c)
$$\begin{array}{r} 15 \\ -28 \\ \hline -13 \end{array}$$

$$\begin{array}{r} 15 \\ +71 \leftarrow \text{9's COMP. OF 3} \\ \hline 86 \rightarrow -13 \end{array}$$

NO CARRY >>> NEGATIVE RESULT

$$86 - 99 = -13$$

BCD SUBTRACTION

RECALL FOR DECIMAL SUBTRACTION:

$$A - B = A + [9\text{'s COMPLEMENT OF } B]$$

- **SIMILARLY FOR BCD**

RULES:

- (a) **ADD 9's COMP. OF B TO A**
- (b) **IF RESULT > 9, CORRECT BY
ADDING 0110**
- (c) **IF MOST SIGNIFICANT CARRY
IS PRODUCED [i.e. =1] THEN
THE RESULT IS POSITIVE AND
THE END AROUND CARRY MUST
BE ADDED.**
- (d) **IF MOST SIGNIFICANT CARRY
IS 0 [i.e. NO CARRY] THEN THE
RESULT IS NEGATIVE AND WE
GET THE 9's COMP. OF THE RESULT**

E.G. $8 - 3 = 8 + [9\text{'s COMP. OF } 3]$
 $= 8 + 6$

$$\begin{array}{r}
 1000 \\
 \underline{0110} \\
 1110 \rightarrow \text{INVALID } (>9) \\
 \underline{0110} \rightarrow \text{CORRECTION} \\
 (1) \ 0100 \\
 \begin{array}{c} \text{L} \rightarrow \underline{1} \end{array} \rightarrow \text{END AROUND CARRY} \\
 0101 = 5
 \end{array}$$

(b) $3 - 8 = -5$

$$\begin{array}{r}
 0011 \\
 \underline{0001} \\
 0100
 \end{array}$$

NO CARRY >>> NEGATIVE
9's COMP. OF 0100 = 0101 = -5

(c) $87 - 39 >>> 87 + [9\text{'s COMP OF } 39]$

$$\begin{array}{r}
 \begin{array}{cc} 8 & 7 \end{array} \quad \begin{array}{cc} 1000 & 0111 \end{array} \\
 \begin{array}{cc} 6 & 0 \end{array} \quad \begin{array}{cc} \underline{0110} & \underline{0000} \end{array} \\
 \begin{array}{c} \text{---} \rightarrow \end{array} \begin{array}{cc} 1110 & 0111 \end{array} \\
 \text{INVALID} \quad \begin{array}{cc} \underline{0110} & \end{array} \\
 \begin{array}{cc} (1) & 0100 \end{array} \quad \begin{array}{cc} 0111 & \end{array} \\
 \begin{array}{c} \text{L} \rightarrow \underline{1} \end{array} \\
 \begin{array}{cc} 0100 & 1000 \end{array} \\
 = \quad \quad \begin{array}{cc} 4 & 8 \end{array}
 \end{array}$$


(d) $18 - 72 \ggg 18 + [27]$

0001	1000	
0010	0111	
0011	1111	→ NO CARRY NEGATIVE
0001	0110	
0100	(1) 0101	← CORRECTION
4	5	= -54

OUTPUT IS A **NEGATIVE** NUMBER >>
THE RESULT IS IN **9's COMP.** FORM

(e) $65 - 12 \ggg 65 + [87]$

0110	0101	
1000	0111	
1110	1100	→ INVALID
0110	0110	CORRECTION
(1) 0100	(1) 0010	
<div style="text-align: right; border-bottom: 1px solid black;">1</div> <div style="text-align: right;">0101</div>	<div style="text-align: right; border-bottom: 1px solid black;">1</div> <div style="text-align: right;">0011</div>	END AROUND CARRY
5	3	

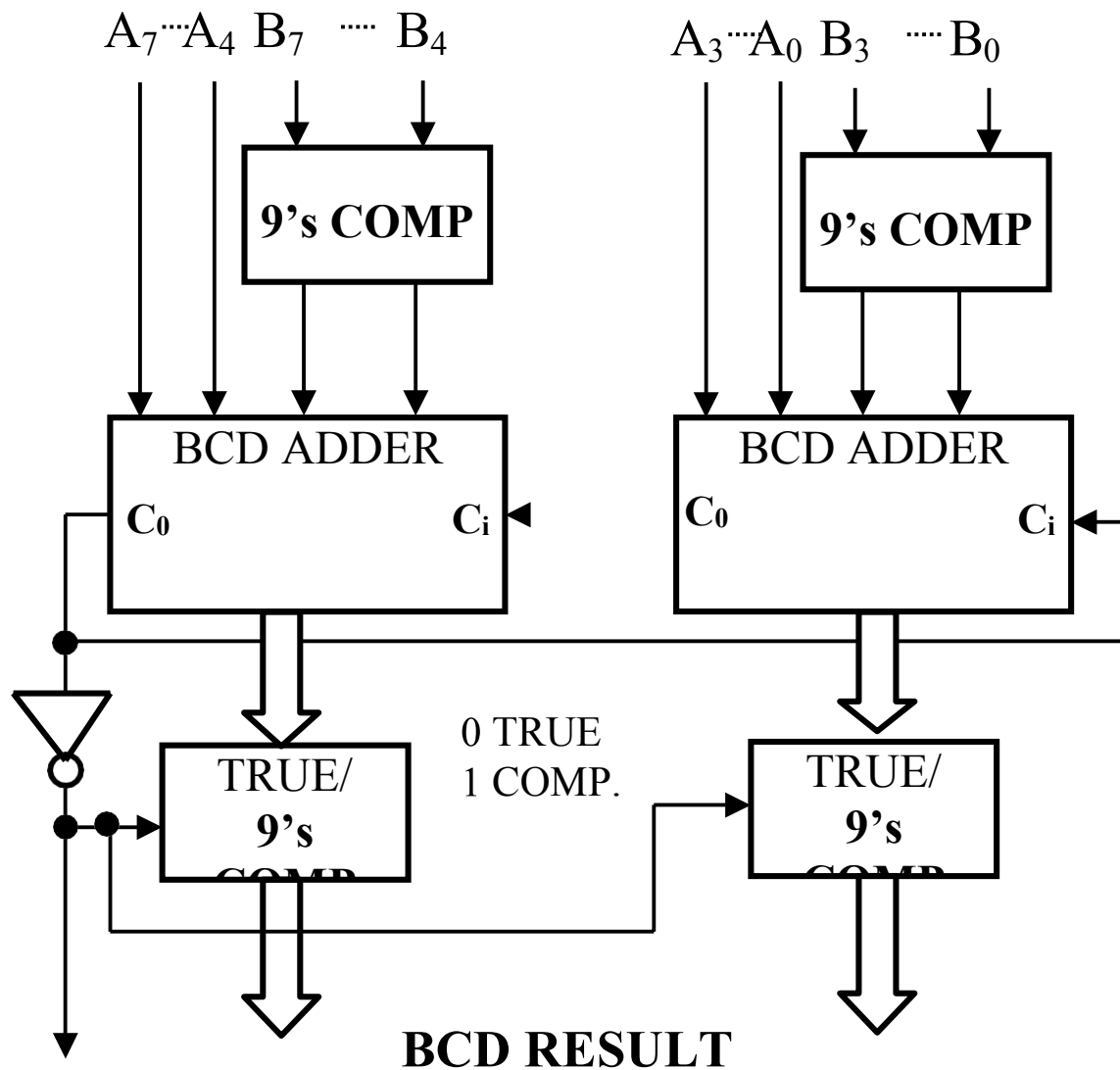

SIGN:
 0 POSITIVE
 1 NEGATIVE

9's COMPLEMENT

9's COMPLEMENT OF A NUMBER
= 9 – NUMBER

BUT SUBTRACTORS ARE NOT WIDELY AVAILABLE >>> **WE GENERATE THE 9's COMPLEMENT BY ADDING 1010 TO THE INVERTED NUMBER**

BCD DIGIT	$\overline{\text{DIGIT}}$	$\overline{\text{DIGIT}} + 1010$ = 9's COMP $C_3 C_2 C_1 C_0$
0 0 0 0	1 1 1 1	1 0 0 1
0 0 0 1	1 1 1 0	1 0 0 0
0 0 1 0	1 1 0 1	0 1 1 1
0 0 1 1	1 1 0 0	0 1 1 0
0 1 0 0	1 0 1 1	0 1 0 1
0 1 0 1	1 0 1 0	0 1 0 0
0 1 1 0	1 0 0 1	0 0 1 1
0 1 1 1	1 0 0 0	0 0 1 0
1 0 0 0	0 1 1 1	0 0 0 1
1 0 0 1	0 1 1 0	0 0 0 0

WE IGNORE THE CARRY OUT